

Processor implementation

the big picture

processor has two main parts:

- **datapath**: carries out arithmetic and other operations, moves operands and results around
- **control**: selects, activates, sequences activities within the datapath

execution of a machine language instruction is broken up into **steps**; each step takes a single clock cycle to complete

... and so, the end of a clock cycle must cause one step to end, and a new step to begin, but **how**?

use **storage elements** (e.g. PC, other registers) that are implemented in such a way that the **stored values can change only at the end of a clock cycle**

Sequential circuits


(reference: text Sections A.7, A.8, 4.2)

circuits we've seen so far have been **combinational** circuits, whose output is purely a function of the current input

the output of **sequential** circuits depends both on the current input, and on the current circuit “**state**” (value stored), as set by previous inputs

S-R latch

(from text Fig. A.8.1)

 

stored value is given by **Q** output

when **S = 1, R = 0**, stores a **1**


when **S = 0, R = 1**, stores a **0**

when **S = 0, R = 0**, **no change** to the stored value

... how do we figure this out?

D latch

(from text Fig. A.8.2)

 


when $C = 0$, no change to the stored value

when $C = 1$, stores the D input value

D flip-flop

(from text Fig. A.8.4)

 


the **D** input value is stored **only** when the clock input **C** transitions from **1 to 0**, marking the **end of a clock cycle** and the beginning of the next

can build a 32-bit register whose contents can change only at the end of a clock cycle, using 32 of these D flip-flops

A simple, single clock cycle datapath

(reference: text Sections 4.1, 4.3, 4.4)

 start with a datapath that can only execute the RISC-V “add”, “sub”, “and”, and “or” instructions (we have designed an ALU that can perform these operations)



includes: PC, adder, instruction memory, “register file”, ALU

why is this a “single clock cycle” datapath?

for these operation times: memory - 2 ns, ALU - 1 ns, adder - 1 ns, register file (read or write) - 0.5 ns, how long would the clock cycle time need to be?

why do we need a separate adder, instead of just using the ALU to add 4 to the PC?

datapath enhancements to support “lw”/“sw” and “beq”

initial datapath supported only R-type format instructions; “lw” uses the I-type format, “sw” uses the S-type format, and “beq” uses the B-type format

lw/sw

31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0
Imm[11:0] | rs1 | funct3 | rd | opcode
(12 bit immediate)

31 30 29 28 27 26 25 24 23 22 21 20 19 18 17 16 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1 0
imm[11:5] | rs2 | rs1 | funct3 | imm[4:0] | opcode
(bits 5 to 11 of 12 bit immediate) (bits 0 to 4 of 12 bit immediate)

need a “data memory”

- add data memory component, with read/write control lines

need to form a 32-bit immediate operand

- add “immediate generation” unit

need to use as one of the inputs to the ALU the immediate operand rather than a second register

- add **new multiplexor**

for “lw”, need to write the word that was read from memory into a register, rather than the result of the ALU operation as with the R-type instructions

- add **new multiplexor**

for “sw”, need to disable writes into register file

- add **“write control line”**

(from text Fig. 4.10)

